



UNIVERSITY
IYUNIVESITHI
UNIVERSITEIT

E344 Assignment 8

Zaskia Van Zyl

22569650

Report submitted in partial fulfilment of the requirements of the module
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical
and Electronic Engineering at Stellenbosch University.

October 17, 2022

Plagiaatverklaring / Plagiarism Declaration

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

Plagiarism is the use of ideas, material and other intellectual property of another's work and to present is as my own.

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

I agree that plagiarism is a punishable offence because it constitutes theft.

3. Ek verstaan ook dat direkte vertalings plagiaat is.

I also understand that direct translations are plagiarism.

4. Dienooreenkomsdig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelikse aanhaal van teks sonder aanhalingsstekens (selfs al word die bron volledig erken) plagiaat is.

Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.

22569650	
Studentenommer / Student number	Handtekening / Signature
Z. Van Zyl	October 17, 2022

Voorletters en van / Initials and surname

Datum / Date

Contents

Declaration	i
List of Figures	iv
List of Tables	vi
Nomenclature	vii
1. Literature survey	1
1.1. Operational amplifiers	1
1.2. Current sensing	1
1.3. Ultrasonic Range sensor	2
1.3.1. Converting PWM signals to analogue	2
1.3.2. Fundamental operation of the range sensor	2
1.4. Converting digital values to analogue equivalents	4
2. Detail design	5
2.1. Current sensor	5
2.2. Analogue range sensor	6
2.3. Digital to Analogue converter	6
2.4. Voltage Regulator	8
2.4.1. 5V Voltage Regulator	8
2.4.2. 3.3V Voltage Regulator	8
2.4.3. Design of System	9
2.5. Motor control	9
2.6. PWM control and Range sensor	11
2.7. Current Sensor	11
2.8. Low-side Switch	11
2.9. Battery charging	12
2.9.1. Voltage regulation	12
2.9.2. High side switch	13
2.9.3. Current limit	14
2.10. Battery Protection	15
2.11. Load	16
2.11.1. Low-side switch	16
2.12. Bluetooth Serial Interface	16
2.13. GUI PC software	18

3. Results	19
3.1. 5V Regulator	19
3.2. Current Sensor	20
3.2.1. Simulated results	20
3.2.2. Measured results	20
3.3. Analogue Range Sensor	21
3.4. Digital to analogue converter	22
3.4.1. Simulated results	22
3.4.2. Measured results	22
3.5. Motor Control	23
3.6. Control of the Left wheel	24
3.6.1. Simulated results	24
3.6.2. Measured results	25
3.7. Battery protection	25
3.7.1. simulated results	25
3.7.2. Measured results	25
3.8. Lead-acid battery results	26
3.8.1. Simulated results	26
3.8.2. Measured results charger	26
3.9. Bluetooth Serial Interface	27
3.10. GUI Results	27
4. Physical implementation	29
Bibliography	32
A. Social contract	33
B. GitHub Activity Heatmap	34

List of Figures

1.1.	Movement of sound from and to the sensor. [?]	2
1.2.	Ultrasonic sensor HC-SR04	3
1.3.	weighted summing amplifier [?]	4
2.1.	Circuit that is implemented	5
2.2.	Analogue range sensor circuit	6
2.3.	DAC simulated circuit	7
2.4.	5V Regulator Schematic [?]	8
2.5.	3.3V Voltage Regulator Schematic [?]	9
2.6.	System Design Diagram	9
2.7.	Motor Control Circuit	10
2.8.	Driver Circuit	11
2.9.	System Design Diagram	12
2.10.	Circuit schematic of the voltage regulator	13
2.11.	Circuit schematic of high side switch	14
2.12.	Circuit schematic of the total battery charging circuit	15
2.13.	high side switch and schmitt trigger	16
2.14.	Under voltage protection circuit	17
2.15.	code used to establish Bluetooth connection	18
2.16.	code to determine the distance from the sensor	18
2.17.	The layout of the interaction of the system	18
3.1.	Output of 5V Regulator	19
3.2.	Output of 5V adnd 3.3V Regulator	19
3.3.	simulated output of current sensor	20
3.4.	Measured output of current sensor	21
3.5.	Ultrasonic sensor simulation circuit	21
3.6.	Simulation of the Analogue range sensor, the first figure indicates the step changes and the second figure indicates output at 5cm	22
3.7.	measurements of the Analog range sensor	22
3.8.	DAC simulated circuit	23
3.9.	Output with different voltage inputs	23
3.10.	Output of simulated Motor Control and Driver Circuit	24
3.11.	Simulated results	25
3.12.	Simulated results	26
3.13.	Simulated results	26

3.14. The outputs read form Termite	27
3.15. The outputs produced by the implemented GUI	28
4.1. Picture of circuit and Student card	29
4.2. Picture of circuit and set-up in the labs	29
4.3. Student card and DAC Circuit	29
4.4. A4 circuit	30
4.5. A5 circuit	30
4.6. Under Voltage circuit	31
4.7. Battery charger circuit	31

List of Tables

1.1.	Different results expected to at different inputs	4
2.1.	Different results expected to at different inputs	7
2.2.	Final Resistor values	10
2.3.	Chosen resistor values	12
2.4.	Schmitt trigger values that needs to be considerd	15
3.1.	outputs for different load inputs	20
3.2.	Different results measured at different inputs	23
3.3.	Voltage Outputs of Motor Control Circuit	24
3.4.	Output values of the analogue circuit	25
3.5.	Measured results for under voltage protection	25
3.6.	Output values	27

Nomenclature

Variables and functions

V	Voltage
I	Current
A	Ampere
R_f	eedback resistor
V_{ref}	Reference Voltage
f_o	roll off frequency
V_{ref}	Reference Voltage
V_{TH}	High threshold Voltage, Schmitt trigger
V_H	High output Voltage, Schmitt trigger
V_{TL}	Low threshold Voltage, Schmitt trigger
V_L	Low output Voltage, Schmitt trigger

Acronyms and abbreviations

KVL	Kirchhoff's voltage law
ESP	Espressif Systems
Op amp	Operational Amplifier
VCVS	Voltage-controlled voltage-source
RC	Resistor-Capacitor
temp	Temperature
PWM	Pulse width modulation
DAC	Digital to Analogue converter
FFT	Fast Fourier transform
MOSFET	Metal Oxide Semiconductor Field Effect Transistor
NMOS	N-channel Metal Oxide Semiconductor
PMOS	P-channel Metal Oxide Semiconductor
ADC	Analog to Digital converter
PSSR	Power Supply Rejection Ratio
MSB	Most Significant Bit
GUI	Graphical User Interface
cmd	Command

Chapter 1

Literature survey

1.1. Operational amplifiers

Operational amplifiers: limitations and considerations

Operational amplifiers have a few limitations. The supply voltage must range between 1.8V and 5.5V. If the max supply voltage is exceeded the op amp will fail. The input voltage range is limited to $V_{SS}-1V$ and $V_{DD}+1V$. The op amp is limited by rail-to-rail voltage a positive of 5.5V voltage and a negative is taken as a zero voltage from ground. Making use of rail-to-rail voltage gives us more control to work with. The op amp also has a maximum acceptable common mode voltage that provides limitations that need to be abide by. An operational amplifiers slew rate, the maximum rate of the output voltage over time, provides limits because to provide some stability at high frequencies it has internal frequency compensation.

that is due to the internal frequency compensation that is included in the op amp to provide stability at high frequencies. .

Operational amplifier configurations

Small signals can be amplifier by using a Low-, High- and a Band-pass operational amplifier. Each filter has there personal uses. Band-pass filter out signals outside the bandwidth that is being looked at, Low-pass filters out the signal above a certain frequency and the High-pass does the opposite only filtering out the signals below a certain frequency.

For this project we are working with signals above 1kHz therefor we need to use a Low-pass filter.

1.2. Current sensing

To be able to implement current sensing in a circuit it should be established what is needed.

Invasive sensing makes use of sense resistors as well as probes while non-invasive sensing does not

The difference between low-and high-side sensing is the placement of the resistor. Low-side sensing places the current sensing resistor between the grounds of the load and the power supply. High-side sensing places the shunt resistor between input of the load and the positive terminal of the power supply.

The advantage of low-side sensing is that is it much cheaper than than of high-side sensing.

1.3. Ultrasonic Range sensor

1.3.1. Converting PWM signals to analogue

PWM is changed to DAC voltage. DAC output is generate by the pulses that is used as an input into the Sallen-key filter. The duty cycle was varied by the application of the following equation. [?]

$$DAC = (DutyCycle) \times (A) \quad (1.1)$$

A pulse signal is received that has very prominent DC value as well as noise. The DC value is used by applying a low-pass filter that has the ability to filter out the noise that exceeds a certain frequency. To make sure that the best possible amount of noise is being filtered out the a value for the frequency is chosen. This value is usually very low to ensure the best results are achieved falling in between 1.5Hz and 10Hz .

A second order Sallen-Key low pass filter is an active filter that was used because this filter has the ability to effectively rejects noise as well as apply a non-inverting gain. A VCVS design is created due to the use of 2 resistors and a non-inverting op-amp providing a Sallen-key filter with the ability the be cascaded due to the the high input impedance, stability and the low output impedance.

1.3.2. Fundamental operation of the range sensor

An ultrasonic sensor produces a "chirp" that is used to measure the distance of an object by measuring the amount of time that passes until the sound produced by the sensor has bounces off an object and been received by the sensor again.

$$x = \frac{t \times 343}{2} \quad (1.2)$$

Where t is time in seconds, x is the distance and 343 represents the speed of sound at room temp.

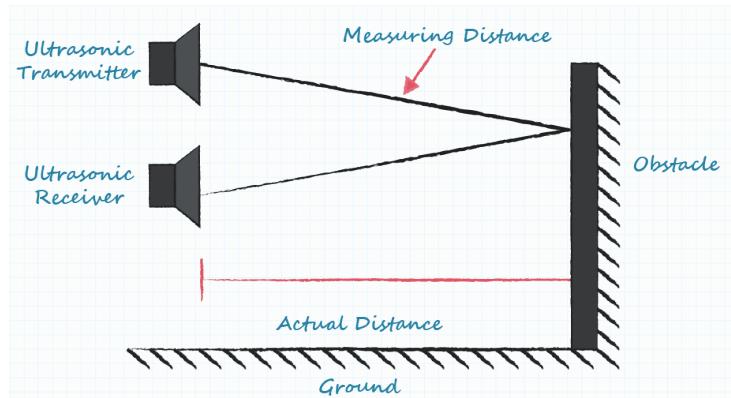


Figure 1.1: Movement of sound from and to the sensor. [?]

The sensor used in the physical build is the HC-SR04. This means that there are a few values that should be taken into account. The working sensor works at the following values $5V$, $15mA$, $40Hz$. The maximum range that the sensor works at is $4m$ and the smallest range the the filter can function at is $2cm$. The sensors accuracy can range to $3mm$. [?]

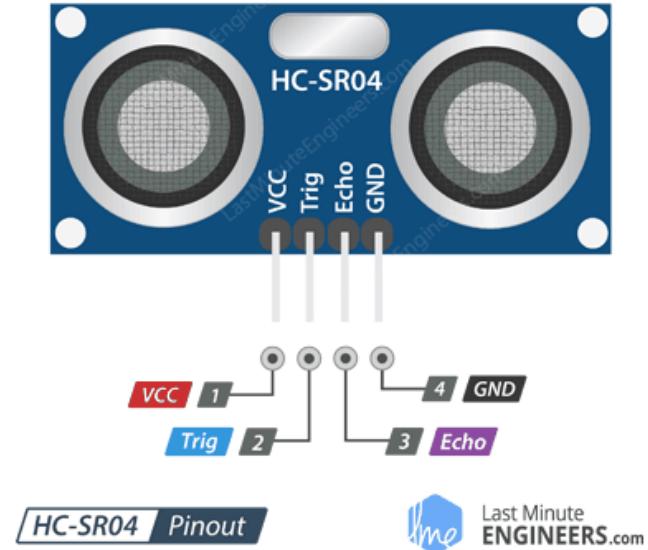


Figure 1.2: Ultrasonic sensor HC-SR04

[2] The sensor the 4 pins that can be used. The V_{cc} is the pin that is used to give power to the ultrasonic sensor. This is where the $5V$ input will be connected from the Arduino board. The Trig pin is where the sound pulse will be triggered from providing the ultrasonic sound chirps to be able to find the object in range when it is set as a high. The Echo pin will fall to a "low" when the sensor receives an echo after it bounced off of an object. The Echo pin will go high as soon as a sound "chirps" is transmitted and will go low if an echo is received. The GND is will be connect to the ground of the Arduino.

The sensor produces 8 pulses at $40KHz$ when the trigger pin has been set as high of $10\mu s$ and the Echo pin is set High. The only reason why 8 pulses it transmitted is to ensure that the sensor can correctly identify the echo of the signal and not just pic up other external ultrasonic sounds. When there is no pulse that is received after is bounced off an object in range the echo signal will go back to low after $38ms$. In the case that the 8 pulses are received back to echo pin will go back to low at the moment that the signal has been received. The echo pin will then generate a pulse that can have a pulse width anywhere between $150\mu s$ and $25ms$.

The distance can then be determined by the period of the signal that has been received by the echo pin. The larger the width of the wave the larger the distance from the sensor and the higher the voltage of the circuit. In the practical the trigger transmits every $60ms$ and produces a $10\mu s$ wave.

1.4. Converting digital values to analogue equivalents

A summing amplifier is used to convert digital values to analogue values.

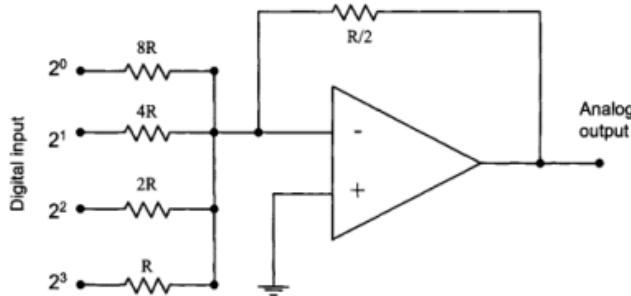


Figure 1.3: weighted summing amplifier [?]

A summing amplifier is used to convert the given digital signals to analogue signals. An inverting and non-inverting amplifier has a very big impact on the system. [1]

Inputs	0000	1111
Expected outputs	>3V	<0.5V

Table 1.1: Different results expected to at different inputs

When we take these results into consideration it can be seen that the best option is to make use of seeing as the high inputs produces lower input. [2]

The amplifier supplied by an average voltage. The average voltage is the common mode voltage to the op-amp. The input voltages of the operational amplifier is limited seeing as the rail-to-rail element of the op-amp limited to the supplied voltage. The operational amplifier can be damaged if the input voltage is not limited by the supplied voltage.

All the inputs produces an output that can range from 0V and 3.3V. R_f is used as the feedback resistor that bias at a zero-potential the inverting operational amplifier.


A 4-bit binary number can produce number that range between 0 – 15. A binary code 8 – 4 – 2 – 1 will receive a result of 2^0 , 2^1 , 2^2 and 2^3 .

The impedance input as well as output is an important aspect when it comes to deigning the circuit for instance we want a high input impedance but a low output impedance. This makes it possible to ensure that the the maximum expected current is delivered and that the load effect can be eliminated as best possible.

Chapter 2

Detail design

2.1. Current sensor

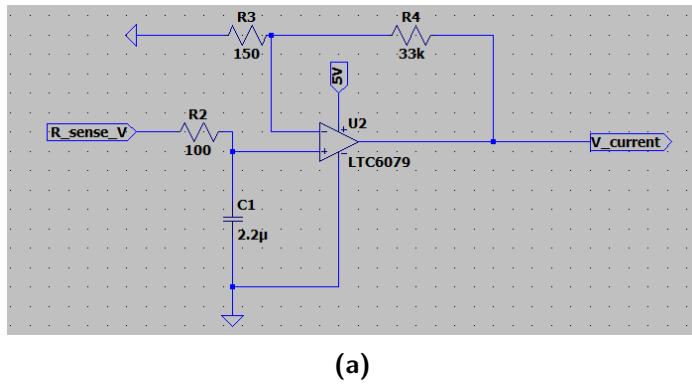

(a)

Figure 2.1: Simulated circuit [1].

An active low pass filter is used to amplify the input to the op amp. This is used to filter out some of the unwanted noise in the system. The noise can be seen as a voltage source that is applied. To design our circuit we chose 2 resistor values and designed the other.

When designing the circuit one of the most important consideration were the maximum flow of current that could occur is in worst case. This is measured by stalling the motor when the current being drawn by the motor has stabilized. This is measured as 1.25A at stall and 0.1 at the stabilized state. R_{SenseV} is calculated as

$$R_{SenseV} = I_{DC} \cdot R_{Sense}. \quad (2.1)$$

After calculating the R_{SenseV} the gain can be calculated by.

$$G(Gain) = \frac{\Delta Output}{\Delta Input} = \frac{3 - 0.1}{0.0125} = 232. \quad (2.2)$$

The capacitor value can now be calculated by

$$C1 = \frac{1}{(2\pi)(R3)(f)} = \frac{1}{(2\pi)(100)(1000)} = 1.6 \times 10^{-6} F. \quad (2.3)$$

We chose our resistor values as 150Ω and 27000Ω and calculate $R4$.

$$R4 = \frac{R2}{G - 1} = \frac{33000}{232 - 1} = 143\Omega. \quad (2.4)$$

2.2. Analogue range sensor

The sensor needs the following to work properly. It needs a 5V input, 15mA current, 40Hz frequency and the pulse needs to be close to 5V.

The cut-off frequency is picked in this case it is 1.5Hz. The value of R1 and R2 is the same as well as the value of C1 and C2. Resistor are chosen as $12\text{k}\Omega$ and the Capacitor are calculated to be a value of $8.842\mu\text{F}$.

A value of $10\mu\text{F}$ is used because it is the value that comes closest.

A low-pass RC filter is used with a cutt-off frequency of 1.5Hz. R3 is picked to be $22\text{k}\Omega$ and then the capacitor is calculated as $4.82\mu\text{F}$. This gives us a gain of 10.9 if the outut is devided by the input voltage. The circuit never goes past $750\mu\text{F}$.

$$f_c = \frac{1}{(2\pi)(\sqrt{R_1 R_2 C_1 C_2})}. \quad (2.5)$$

$$C = \frac{\frac{1}{(f_c)(2\pi)}}{(\sqrt{R_1 R_2})} = 8.84\mu\text{F}. \quad (2.6)$$

$$f_c = \frac{1}{(2\pi)(RC)} \quad (2.7)$$

$$C_3 = \frac{1}{(2\pi)(R_3)(f_c)} = 4.82\mu\text{F} \quad (2.8)$$

$$G = \frac{V_{Output}}{V_{Input}} = 10.9. \quad (2.9)$$

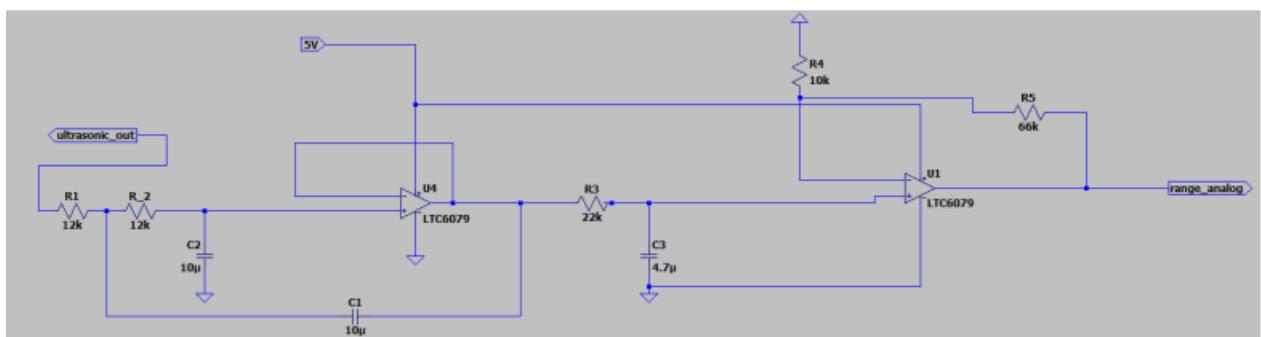


Figure 2.2: Analogue range sensor circuit

2.3. Digital to Analogue converter

A digital to analogue converter is designed to convert the digital input signals that is received to analogue output signals. The DAC is very sensitive to when it comes to input impedance and the circuit has to be protected against it. [1]

The operational amplifier that is used implements rail-to-rail that means that supply voltage will always be limited to 5.5V and have a minimum of 1.8V. This makes it possible for the common-mode voltage to become bigger than the supply voltage while illuminating the possibility that the operational amplifier will be harmed.

A potentiometers is implementer in order to apply further turning to achieve the wanted results.

The source has an output impedance that could if it is not considered have a very big impact on the system.

The input voltages can range between 3.3V and 0V. This is made possible when the DIP-switch is implemented making it easier to apply inputs. 0.5V should be the maximum voltage for an input of 1111 and 3V should be the minimum voltage for a input of 0000.

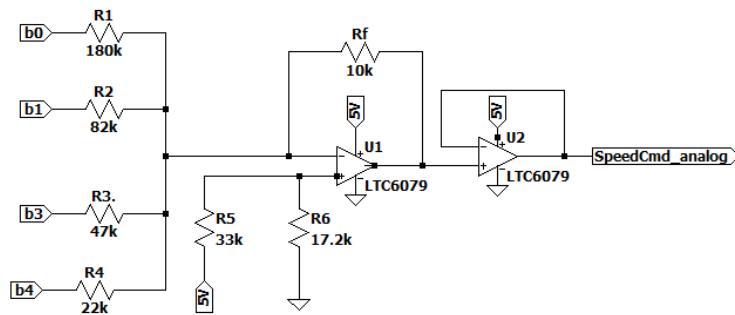


Figure 2.3: DAC simulated circuit

Resistor values used	
R_1	$22\text{k}\Omega$
R_2	$47\text{k}\Omega$
R_3 .	$82\text{k}\Omega$
R_4	$82\text{k}\Omega$
R_5	$17.2\text{k}\Omega$
R_6	$33\text{k}\Omega$
R_f	$10\text{k}\Omega$

Table 2.1: Different results expected to at different inputs

$$V_{out} = \frac{R_f \times V_{b3}}{R_1} + \frac{R_f \times V_{b2}}{R_2} + \frac{R_f \times V_{b1}}{R_3} + \frac{R_f \times V_{b0}}{R_4} \quad (2.10)$$

The resistor values are chosen for R_1 , R_2 , R_3 and R_4 .

For the input of 1111 a V_{out} is picked to be 3.3V. R_f is calculated:

$$R_f = 11733.33\Omega \quad (2.11)$$

To be able to achieve the best output the values are tuned in the simulation but also in the build by implementing a potentiometers. R_f and R_5 .

2.4. Voltage Regulator

A 6V DC battery will supply the system with nominal 7.2V. Seeing as the systems needs a 3.3V and a 5V input voltage regulators are used to be able to supply the correct amount voltage to the circuitry.

2.4.1. 5V Voltage Regulator

A voltage regulator is needed to convert the battery voltage to 5V. The regulator used for this is, is the LD1117 Voltage Regulator. The structure of the circuit can be seen in figure xx. When looking at the schematic, the only component value still needed is R_2 . The steps to find this value, can be found in the datasheet of the component. [?] LD1117 is used because it has a very low dropout voltage. It supply's 800mA from 1.1V dropout and 100mA form 1V dropout voltage. This means that it will be able to deliver the needed current even if it is at its minimum dropout voltage.

Equation 2.12 is used to determine the value of R_2 .

$$V_{out} = V_{ref} + \frac{(R_2)(V_{ref})}{R_1} \quad (2.12)$$

$$R_2 = \left(\frac{5}{1.25} - 1 \right) R_1 = 360\Omega \quad (2.13)$$

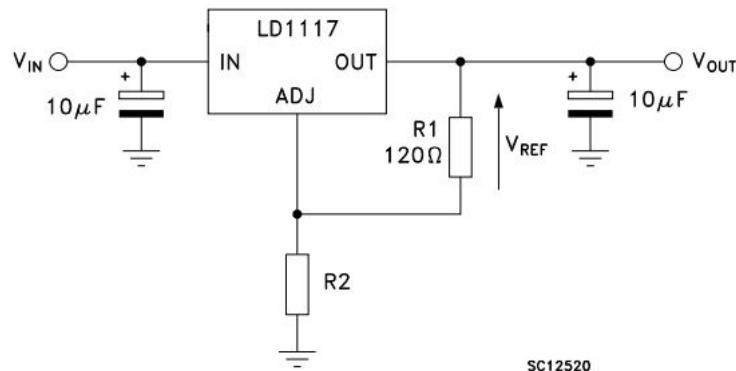


Figure 2.4: 5V Regulator Schematic [?]

2.4.2. 3.3V Voltage Regulator

Various different components in the system use a supply voltage of 3.3V. The LD33CV voltage Regulator is used to provide this. Seeing as the LD33CV is a fixed voltage regulator, the circuit only consists of the regulator component and two capacitors. One with a value of

100nF and another with a value of $10\mu\text{F}$. The schematic seen in figure 2.5 is used as reference when designing and building the circuit. 5V serves as the input voltage. [?]

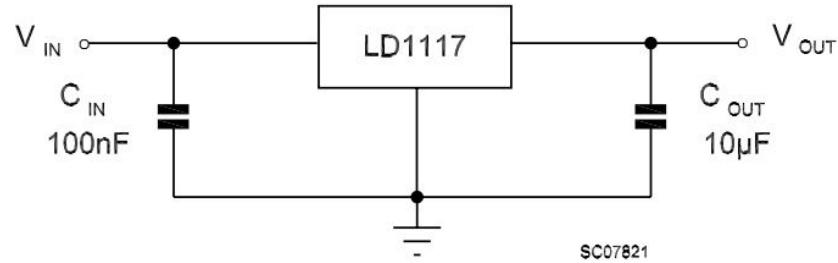


Figure 2.5: 3.3V Voltage Regulator Schematic [?]

2.4.3. Design of System

Figure 2.6 is a diagram of the system design so far.

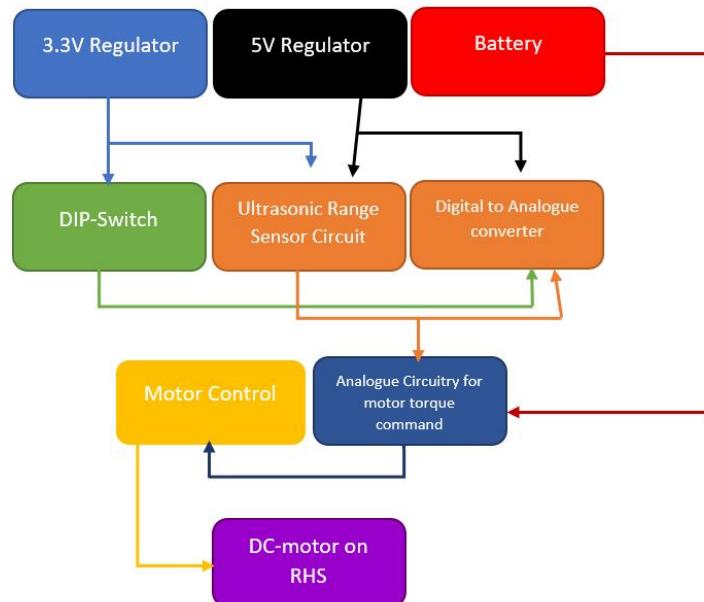


Figure 2.6: System Design Diagram

2.5. Motor control

A op-amp is used to determine the difference between the torque command signal and the output of the range sensor. The given MCP6242 can't supply the needed voltage this means that the TLC2272 op-amp must be used.

The resistor values are chosen with the assumption that unity gain and a balanced bridge is implemented.

$$\frac{R_A}{R_B} = \frac{R_C}{R_D} \quad (2.14)$$

$$V_{out} = \frac{R_B}{R_A} (V_{RANGE} - V_{DAC}) \quad (2.15)$$

2.15 The output of the motor control circuit should be 0V if the Ultrasonic range sensor or the DAC is equal to 3.3V. In the case that the ultrasonic sensor input is 0V and the DAC is 3.3V the V_{range} is equal to zero. In the that the ultra sonic sensor is 3.3V and the DAC input is 0V the V_{DAC} term would just be equal to zero.

$$Gain = \frac{R_A}{R_B} = \frac{7.2}{3.3 - 0.5} = 2.571 \quad (2.16)$$

The rail-to-rail op-amp limits the circuit output to range from 5V to 7.2V creating the need to amplify the input.

Resistor	Value
R_A	10kΩ
R_C	10kΩ
R_B	27kΩ
R_D	27kΩ

Table 2.2: Final Resistor values

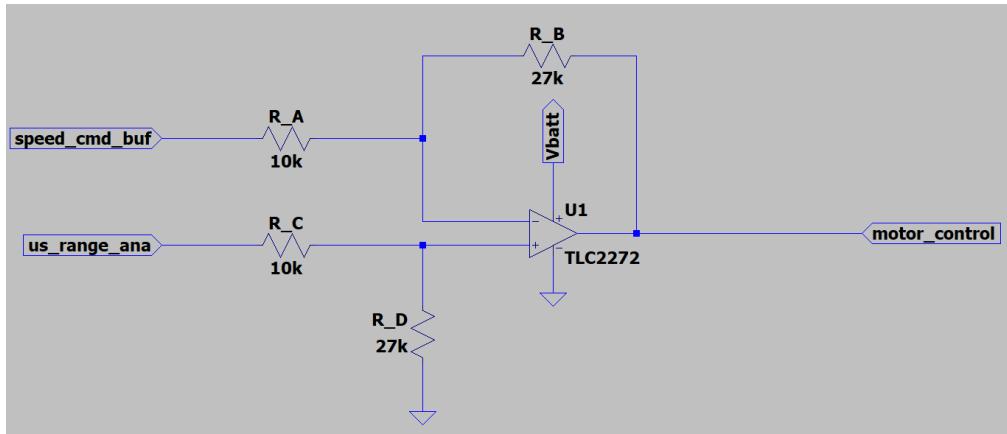


Figure 2.7: Motor Control Circuit

To ensure that the wheel can function a driver circuit needs to implemented. This is done to by implementing the TIP31C to provide current to the DC-motor. A Darlington pair is included to ensure make it possible for the Dc-motor to get high current for higher speeds. The Darlington pair is implemented by using a NPN2N2222A transistor. The Darlington pair will make it possible for the motor the get more current without damaging the rest of the circuit seeing as the other components have current limits. To provide a voltage drop, that is the same as the voltage drop that occurs in the TIP31C if the temperature changes, a LED

and 2 transistor are used to ground the TIP. The driver uses the output of the motor control circuit a input. This can be seen figure 2.8

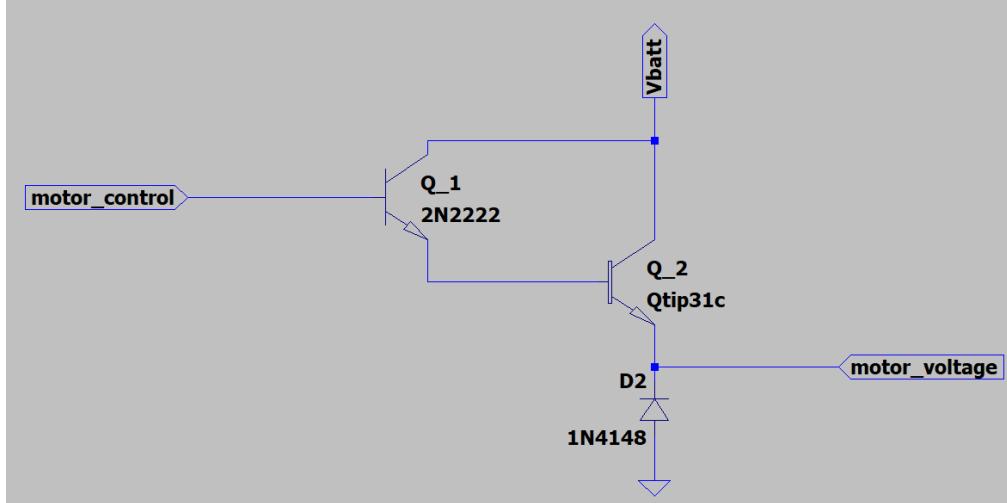


Figure 2.8: Driver Circuit

2.6. PWM control and Range sensor

The right wheel is controlled by a Range sensor using PWM control. The trigger from the sensor is given by the microcontroller. The echo is sent to another pin on the microcontroller. Code is implemented to calculate the distance between an object and the sensor.

The code that has been implemented is included in the ?? . The Dc motor is being driven by the PWM signal and the duty cycle is calculated using eqaution 2.17 .

$$PWMcontrol = speedfact * speedinstru - proximityfact * proximity \quad (2.17)$$

The maximum range of the sensor is used and the distance of the object is subtracted from the range to successfully calculate the proximity.

2.7. Current Sensor

The current sensor was designed like the current sensor for the left wheel. kHz switching frequency is implemented and the reset of the resistor values was determined through testing making use of the simulation. The values have been consen to implement the best gain for the needed filtering.

2.8. Low-side Switch

The current needs to be control and a low-side switch is implemeted for that purpose.

Resistors	values
R_1	$1k\Omega$
R_2	$440k\Omega$
R_3	$595k\Omega$

Table 2.3: Chosen resistor values

A low-side switch used a MOSFET. In the MOSFET needs a VGS-voltage that is below 3.3V. This is to ensure that the micro controller can be used. To be able to drive the motor a minimum needed current to be carried by the MOSFET is 1.5A. Seeing as the MOSFET needs to be grounded a diode as well as a pull-down resistor is implemented as can be seen in 2.9

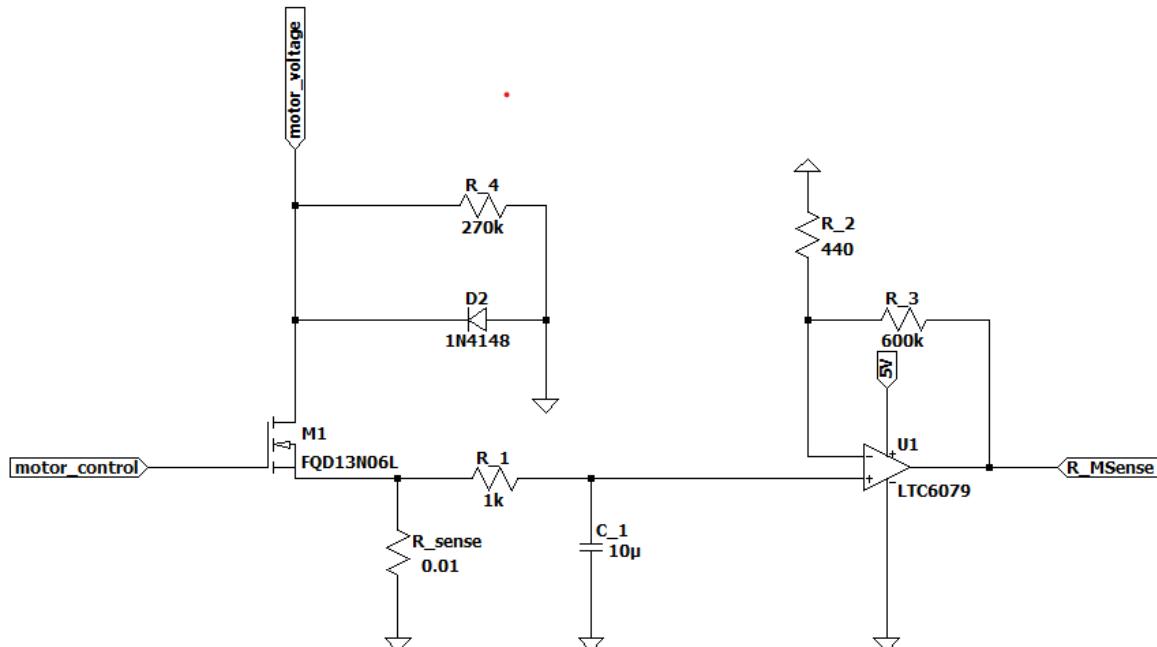


Figure 2.9: System Design Diagram

2.9. Battery charging

2.9.1. Voltage regulation

A linear voltage regulator must be included in the battery. The reason why the voltage regulator needs to be implemented is to be able to remove voltage from the AC/DC adapter or the given input and provide an output that will be able to charge the battery. Figure 2.14 shows the implemented and designed voltage regulator. A voltage of 1.25 V ($V_{ref(reg)}$) will always be over the adjustment and the output pin due the the LM317 data sheet. A (240Ω) resistor was chosen for R_2 because that is what was specified in the data sheet.

The maximum voltage over the battery is when minimal current is flowing to the battery. V_{batt} is chosen as that same value. R_4 is calculated in the equation 2.18. This is done by not taking the R_1 into account and then applying simple voltage division.

V_{batt} will be 7.2 V when at full capacity and 6V when it is fully "flat". This would mean that the voltage between the output and adjoint pin will not always be kept constant at 1.25V. To solve this the regulator will give extra current to R_1 . The addition of current will be increase the voltage over R_1 .

The battery will draw more current to charge. The more the battery charges the higher the V_{bat} becomes until it reaches 7.2 V. When the battery is charged the current will decrease to its original value.

$$R_2 = \frac{R_1(V_{batt} - V_{ref})}{V_{ref}} = 1.14\text{k}\Omega \quad (2.18)$$

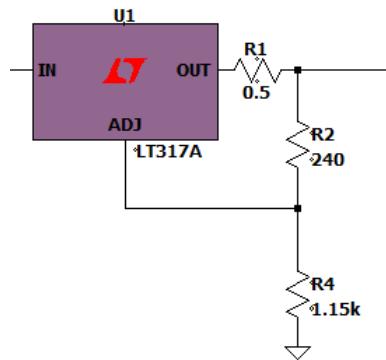


Figure 2.10: Circuit schematic of the voltage regulator

2.9.2. High side switch

The battery can be damaged if it is kept on charge for longer than necessary. To eliminate this problem a switch A high side switch consists of a MOSFETS. The NMOS and a PMOS have different requirement to be able to work. A NMOS needs positive voltage over the gate and the source and a PMOS needs a negative voltage over the gate and the source. These requirement are needed to allow current to flow.

Low side switches makes use of NMOS transistors due to the fact that the NMOS relies on the V_{GS} voltage to allow current to flow. The gate voltage in this case is the same as V_{GS} . The with reference to ground the gate voltage can be controlled and therefore it can act like a switch.

A High side switch is more difficult to control and PMOS transistors work better due to the same logic as the NMOS.

To control the battery charging a high side switch will need to be implemented. A PMOS will be used to create the high side switch that needs to be implemented. Figure 2.11 shows

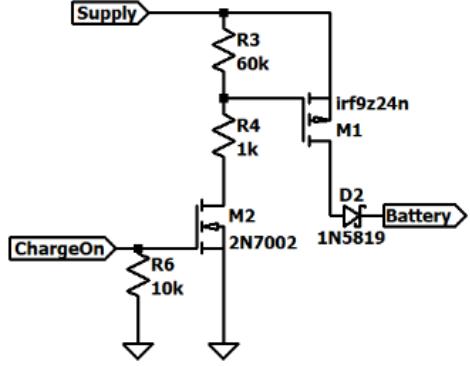


Figure 2.11: Circuit schematic of high side switch

the original design for the high side switch. To ensure that the PMOS is functioning the voltage over the gate and source, V_{GS} , must be greater than that of the threshold voltage, V_{TP} . That means that current has to flow in R4 and R3 that required the NMOS to work properly.

The PMOS needs to be switched on fully, larger V_{GS} , or else power can be wasted. To achieve this R3 has to be much larger than that of R4. After implementing and simulating the circuit in figure 2.11 it was seen that it worked perfectly but on the given PCB there was no space for R4 and therefore it was removed. New values were chosen and implemented. R3 is chosen as $60\text{ k}\Omega$. R_6 is chosen as $10\text{ k}\Omega$ and is implemented to let the charge go to ground as soon as the gate is turned off.

2.9.3. Current limit

R_1 is used to limit the current that is allowed to flow to the battery terminal. The biggest amount of current is drawn when battery is at its lowest in this case it will be at $6V$. 400 mA is the maximum current the will be allowed according to the datasheets. R_1 is calculated by using the following formulas

$$V_{out} = V_{ADJ} + V_{ref(reg)} \quad (2.19)$$

$$V_{ADJ} = \frac{R_2 \times V_{batt}}{R_1 + R_2} \quad (2.20)$$

$$R_1 = \frac{V_{out} - V_{batt}}{I_{max}} = \frac{V_{batt}}{I_{max}} \left(\frac{R_2}{R_1 + R_2} + 1 \right) + \frac{V_{ref(reg)}}{I_{max}} \quad (2.21)$$

$$R_3(\text{Chosen}) = 240.00\Omega$$

$$R_4 = 1.140\text{k}\Omega$$

$$R_1 = 0.50\Omega$$

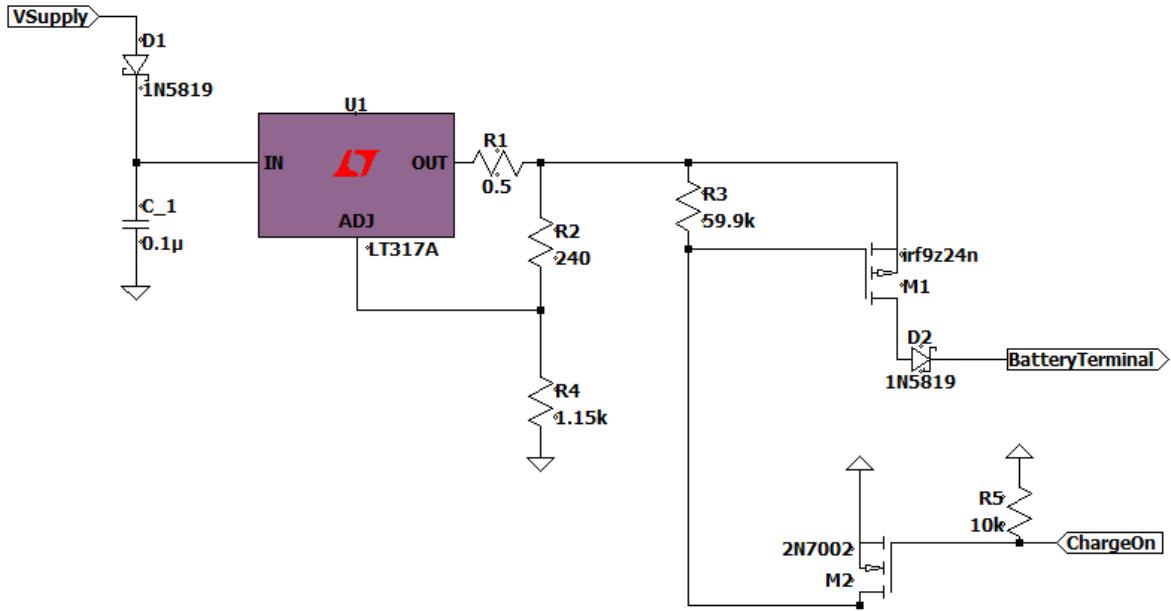


Figure 2.12: Circuit schematic of the total battery charging circuit

2.10. Battery Protection

5V rail-to-rail

The voltage regulator is chosen due to the fact that it has a low drop out voltage. The battery will go as low as 6V and therefore a drop out voltage is very important to consider. To stabilize the regulator a capacitor needs to be added between output pin and the common pin.

High side switch

To stop the current flowing from the battery when the battery is running flat or when V_{bat} is very low a high side switch is implemented. Then current will be allowed to flow if the supply voltage is larger than the voltage of the battery to the battery from the supply. This will happen by making use of a forward body diode voltage. The battery will then start charging.

Designing of the schmitt trigger

Table 2.4: Schmitt trigger values that need to be considered

switch	off	on
Battery voltage	6	6.2
input voltage	3	3.1
output	0.5	4.5
Reference voltage	3.05	3.05

$$V_{ref} = \frac{R_8 V_{in}}{R_7 + R_8} + \frac{R_7 V_{out}}{R_7 + R_8} \quad (2.22)$$

$$V_{ref} = \frac{R_8 V_{TL}}{R_7 + R_8} + \frac{R_7 V_L}{R_7 + R_8} \quad (2.23)$$

$$0.025 = \frac{R_7}{R_8} \quad (2.24)$$

After picking R_7 to be $100\text{k}\Omega$, R_8 can be calculated as $2.5\text{k}\Omega$.

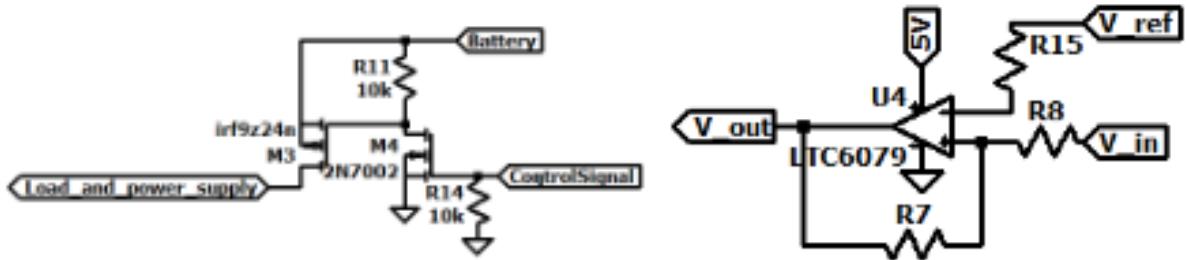


Figure 2.13: high side switch and schmitt trigger

A voltage follower is implemented between the battery and the trigger due to the fact that without it the voltage division could possibly not work as expected.

hysteresis design with hysteresis consideration

2.11. Load

2.11.1. Low-side switch

To be able to control the current flow a NMOS transistor is needed to act like a switch again. This means that it will be able to control the current that is going to flow through the load. The MOSFET used in the low side switch has a Max current from the source of 200mA.

To control the switch a digital 5V will be implemented. This will ensure that the mosfet does not limit the current and the pull down resistor will be implemented to give the charges a place to go when the switch is not on.

This circuit was mostly designed by trial and error. Noting that the r10, Rx and R6 resistor have a very big impact of the output.

2.12. Bluetooth Serial Interface

A state machine as well as a protocol needs to be implemented to be able to see how the code needs to be implemented to be able to get the required results.

Receiving starts in a idle state when it receives a packet of information. This packet contains a pas key that is verified. if the password is seen as correct the length of the packet is identified. The data that has been received is interpreted using the length of the packet

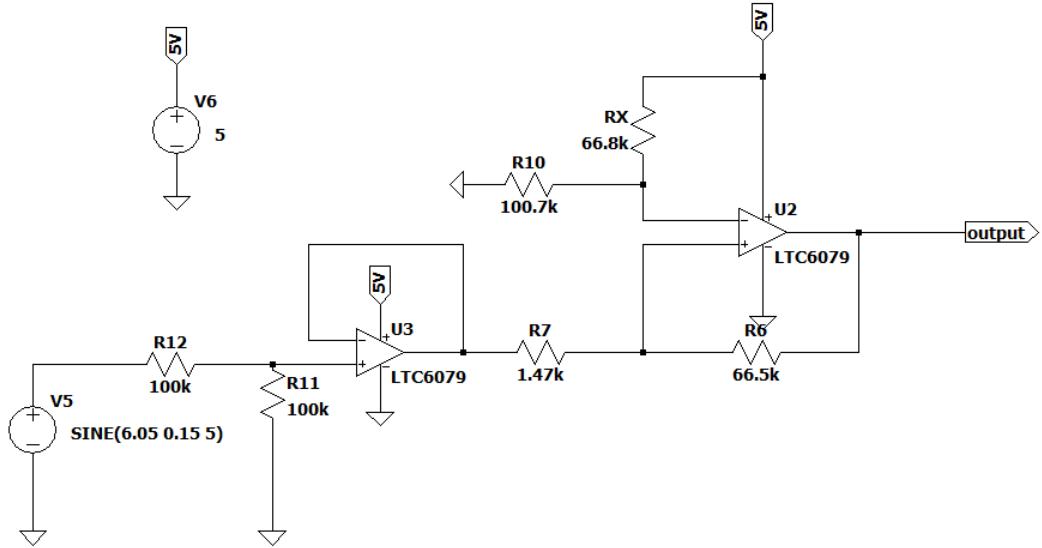


Figure 2.14: Under voltage protection circuit

previously determined. If the data has been received successfully it will return to an idle state.

The commands that are sent are done by first waiting. It receives data that starts to evaluate the received bytes. Based on the bytes a response will be generated that will set or get the needed parameters. After the parameters have been set or gotten the waiting will start again.

The MCU makes use of protocols and receiving packets to be able to interrupt what is asked of it. To be able to communicate the computer sends a code. The code represents a variety of different things. The first byte is the ID key and the second is the Pass key. The 3 represents the Message Id and the rest (X bytes) represents the payload. When the MCU transmits a code back to the computer. The first byte is the payload length. The second represents the message ID and the rest (x bytes) represents the payload.

Protocols and identifiers have been used to help the MCU seen what the computer wants it to do. The information is sent and received in hexadecimal. This makes it easier to transmit and use.

When trying to get the battery voltage a code of XXXX020114 should be used. This just indicates that two bytes are needed, the command is needed and the battery voltage. When trying to set the speed of the wheel to go as fast as possible the following input is needed XXXX030033FF. The 03 represents the needed 3 byte. 00 is the command. The payload shows by 33 that we are working with the left wheel and FF represents the speed.

Instructions are sent with termite. Bluetooth is used by implementing the following code n ?? A serial function is created by enabling the ESP. This connection working like serial communication.

The distance from the object is determined by the formulas implemented in figure 2.16

```
#include "BluetoothSerial.h"

#if !defined(CONFIG_BT_ENABLED) || !defined(CONFIG_BLUEDROID_ENABLED)
#error Bluetooth is not enabled! Please run `make menuconfig` to and enable it
#endif
```

Figure 2.15: code used to establish Bluetooth connection

```
durationRS = pulseIn(echoPinRS, HIGH); //RS PWM
distanceRS = durationRS * 0.034 / 2;
durationLS = pulseIn(echoPinLS, HIGH); //LS PWM
distanceLS = durationLS * 0.034 / 2;
```

Figure 2.16: code to determine the distance from the sensor

Decimal values are used by termite that are then changed binary values. These are the values that are given to bytes that are going to control the function of the wheel.

If the range sensors sees an object in front the car the output bits will be zero leading to the wheels being driven to a zero value. In the case where an object is closer than 1m from the sensor the wheel on that respective side will slow down and eventually stop. Digital Write instruction is used to configure the 4bits that are sent to the Right wheel.

2.13. GUI PC software

A GUI is used to make it easier for the user to make use of as well as understand. In ?? the interaction can be seen.

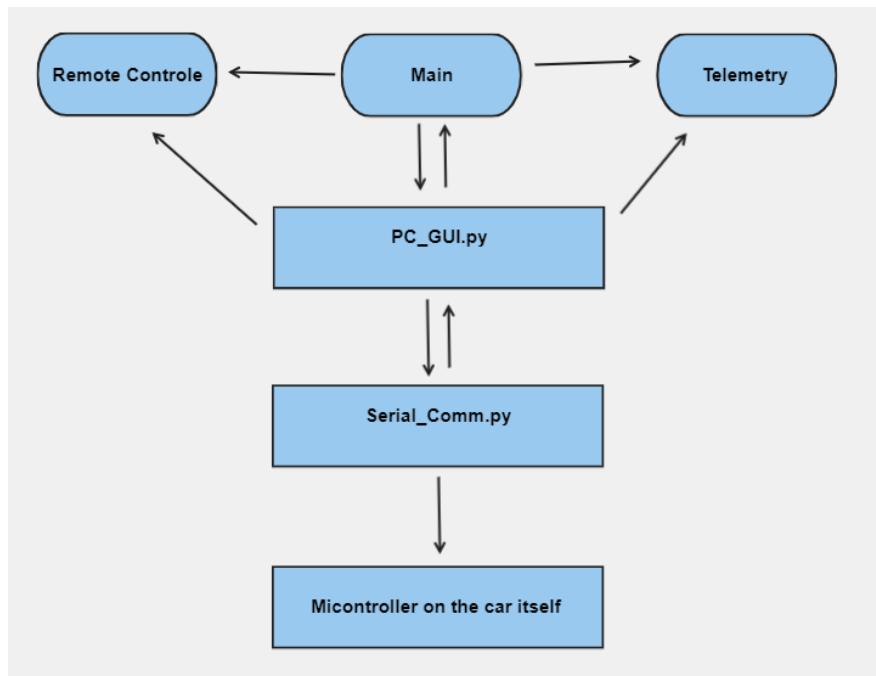


Figure 2.17: The layout of the interaction of the system

Chapter 3

Results

3.1. 5V Regulator

Resistors R_1 and R_2 are chosen as 360Ω and 120Ω respectively. With this in mind, the circuit is built. The results can be seen in figure 3.1.

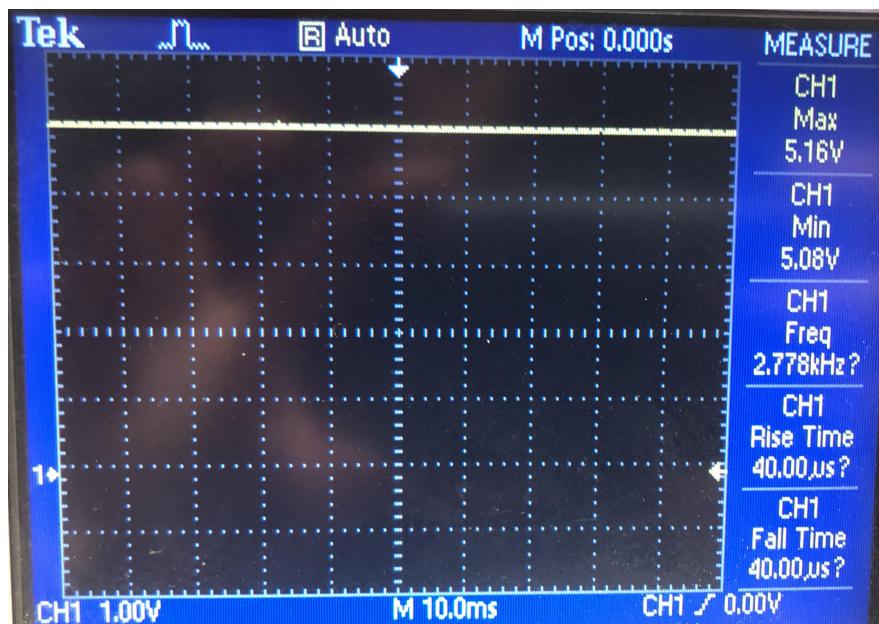


Figure 3.1: Output of 5V Regulator

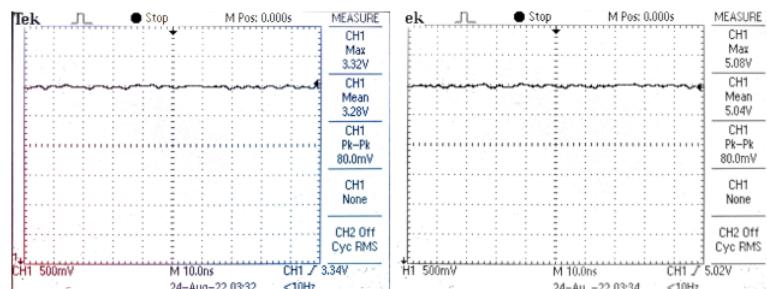


Figure 3.2: Output of 5V adnd 3.3V Regulator

3.2. Current Sensor

3.2.1. Simulated results

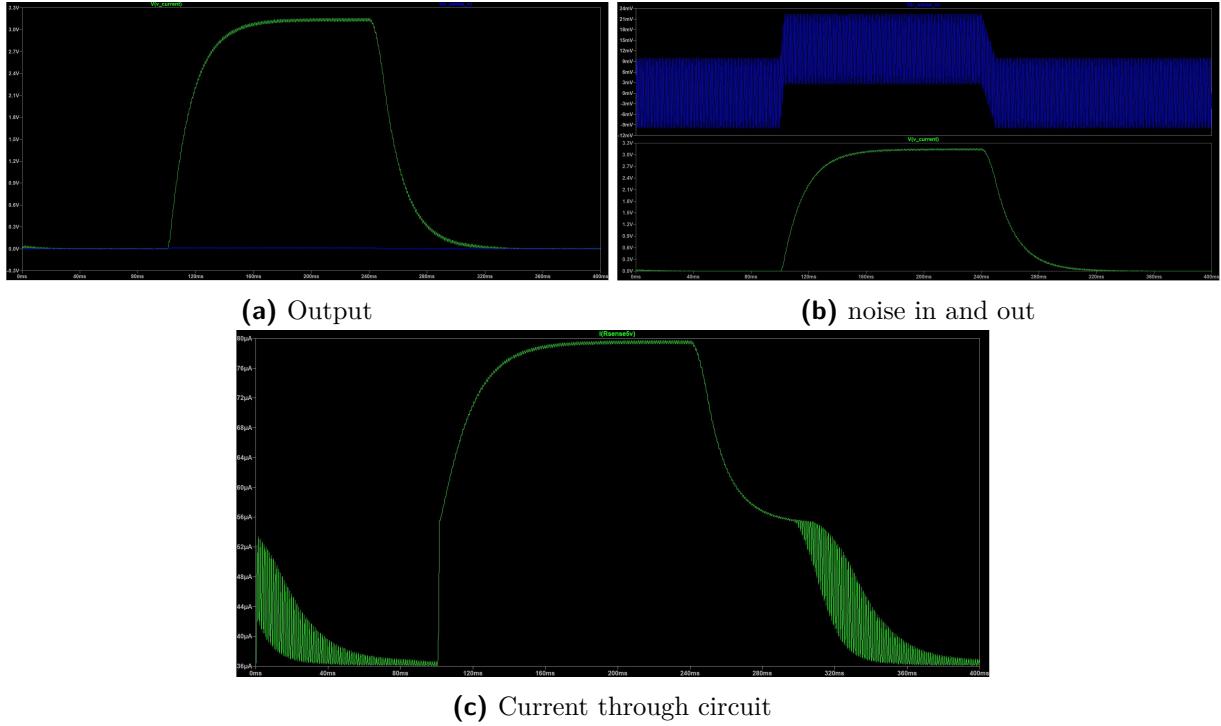


Figure 3.3: simulated output of current sensor

The noise in the 70mv peak-peak range that is allowed.

3.2.2. Measured results

As can be seen in the above figures ?? the simulated and measured results correlate very closely with slight differences that can be due to noise in the system. The response time of the circuit can be seen to be more than good enough if relying on the expected results. The response time is around 900ms. It is very apparent that the closer the object get to the sensor the bigger the voltage gets.

Load	Value
Full load	3.8VΩ
No load	230mVΩ
Slight load	3.8VΩ

Table 3.1: outputs for different load inputs

In the above table 3.1 can be seen that all the obtained values fall within the given specifications.

Simulated voltages are almost double that of the no-load output voltages seeing as the simulated values worked with 200mA and not 100mA that was used in the circuit itself.

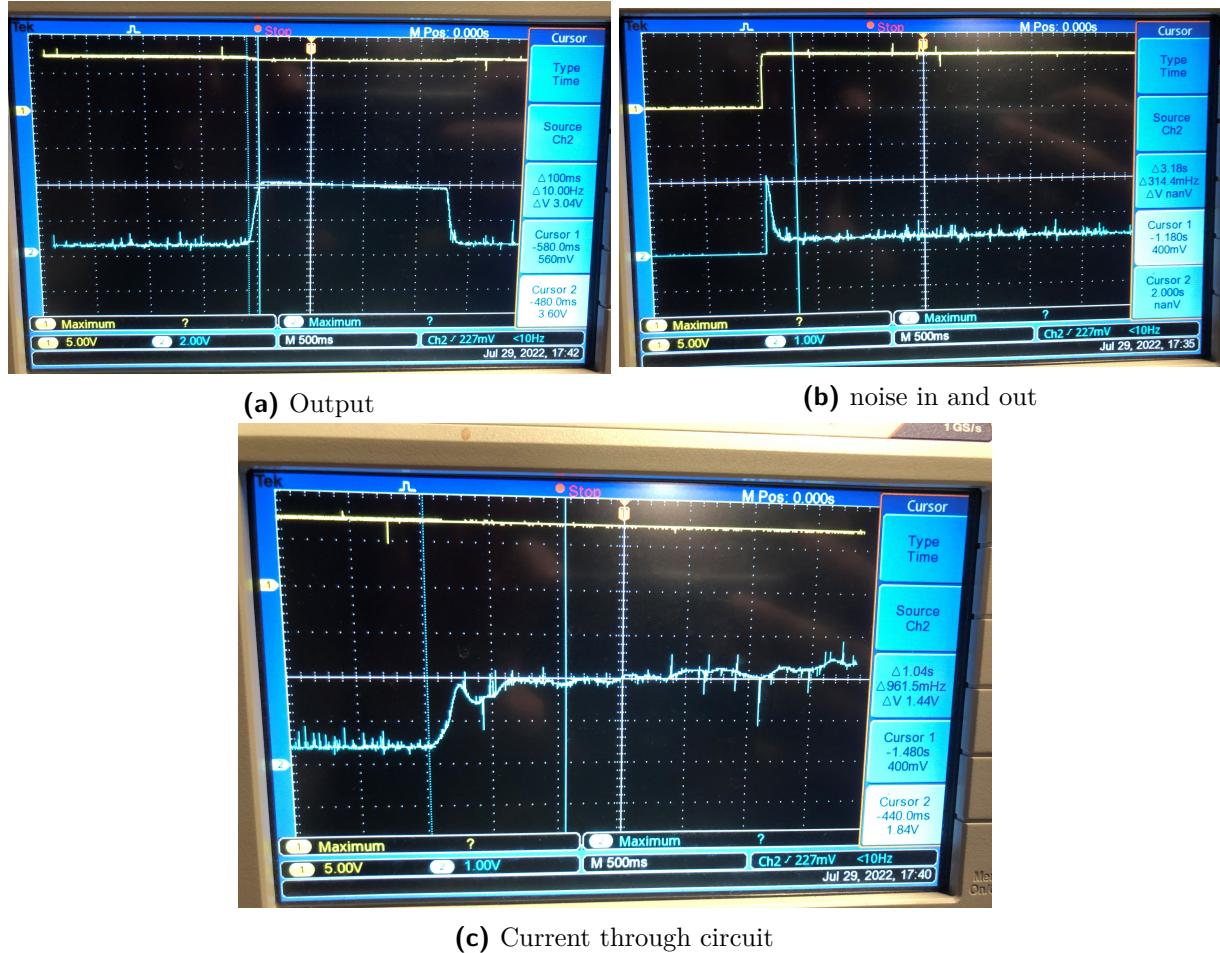


Figure 3.4: Measured output of current sensor

3.3. Analogue Range Sensor

In the figure ?? the ultrasonic circuit can be seen.

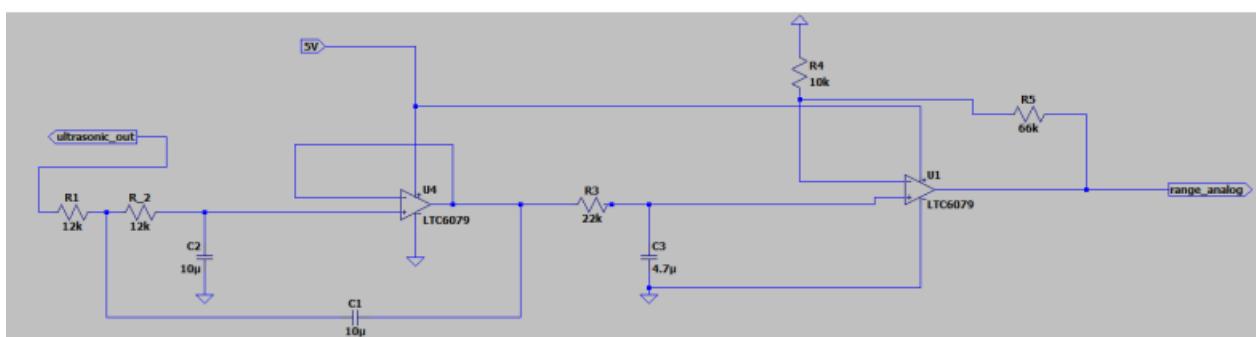


Figure 3.5: Ultrasonic sensor simulation circuit

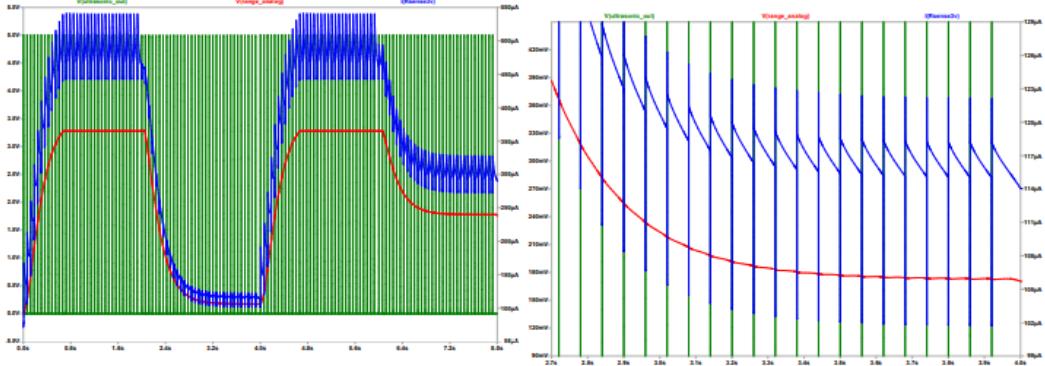


Figure 3.6: Simulation of the Analogue range sensor, the first figure indicates the step changes and the second figure indicates output at 5cm

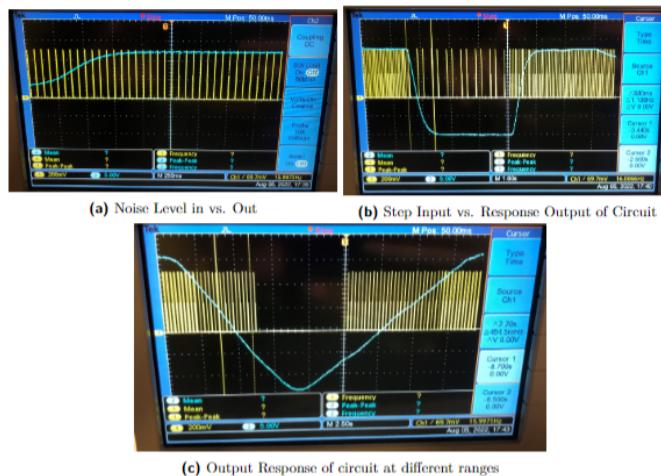


Figure 3.7: measurements of the Analoge range sensor

3.4. Digital to analogue converter

3.4.1. Simulated results

To be able to compensate for the offset of the amplifier an inverting summing amplifier is used with a voltage regulator. This circuit can be seen in Figure ??

The current has a range between $356\mu A$ and $194\mu A$. The voltage output can be seen to fluctuate depending on the input that is given.

3.4.2. Measured results

As expected the different voltage inputs will deliver different outputs.

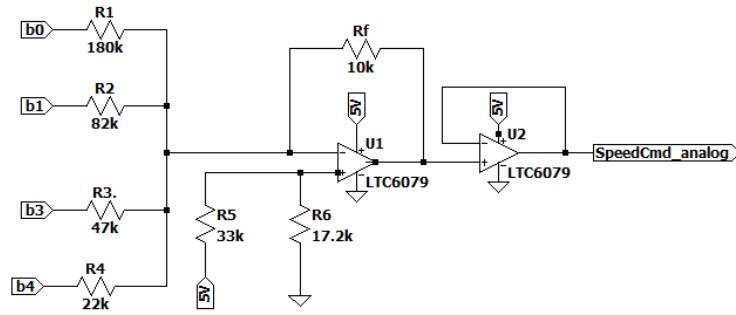


Figure 3.8: DAC simulated circuit

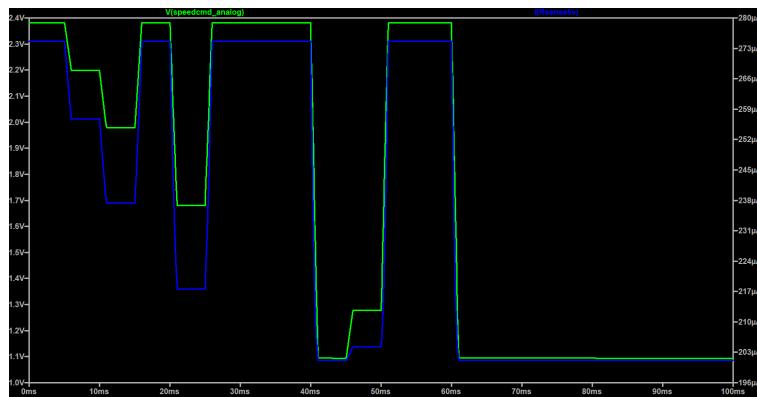


Figure 3.9: Output with different voltage inputs

Inputs	0000	0001	1111	1110
Multiple row	3.25V	3.00V	0.24V	1.74V

Table 3.2: Different results measured at different inputs

3.5. Motor Control

The motor control circuit is simulated and then built, the results can be seen in the figures and table below.

The results of the simulated circuit can be seen in figure xx

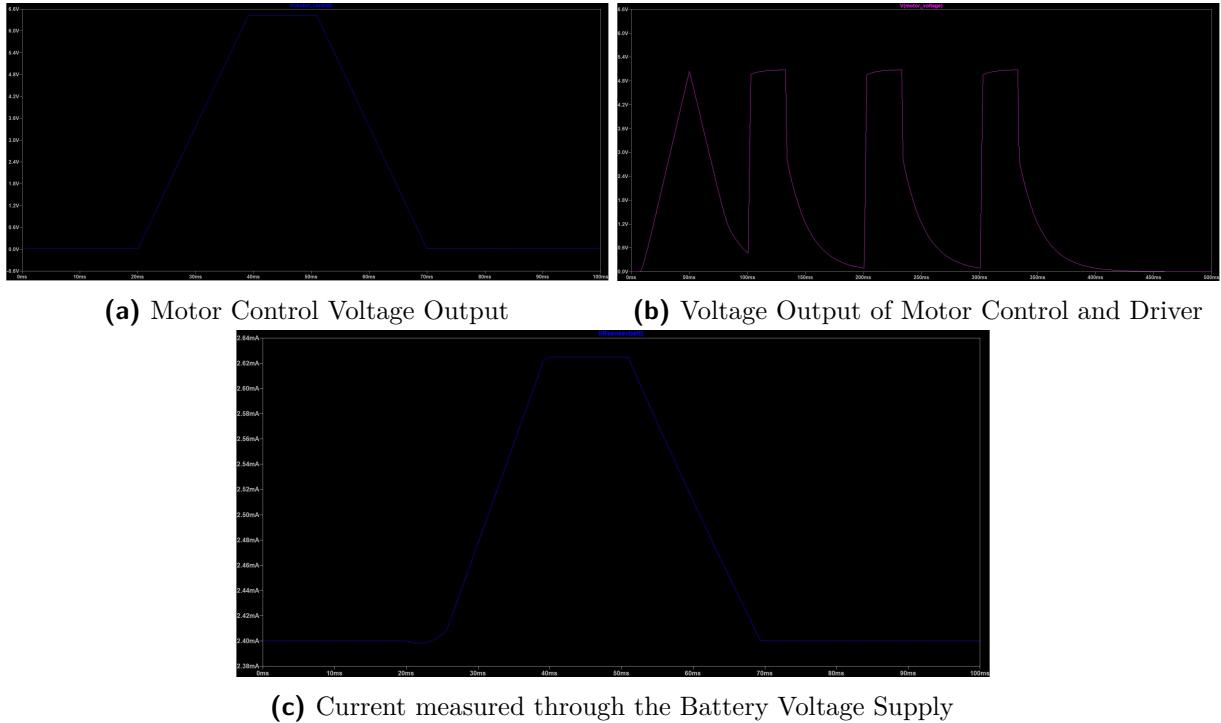


Figure 3.10: Output of simulated Motor Control and Driver Circuit

measured results of current through entire circuit can be seen in table below.

Voltages	Input 0011 (fast)	Input 0001 (slow)
Object is close	0	0
Object is far away	4.24	3.35
No object in front of sensor	5.3	3.36

Table 3.3: Voltage Outputs of Motor Control Circuit

The maximum output voltage is never more than 5.8V due to the implemented darlington pair.

3.6. Control of the Left wheel

The left side wheel is implemented by using the Arduino. A current sense circuit is implemented that includes a gain to be able the communicate with the Arduino and left wheel.

3.6.1. Simulated results

If an object is close to the ultrasonic sensor the voltage output is 1.9V and when the object is father than 1m the voltage is measured at 3.26V.

The simulated results can be seen in ??.

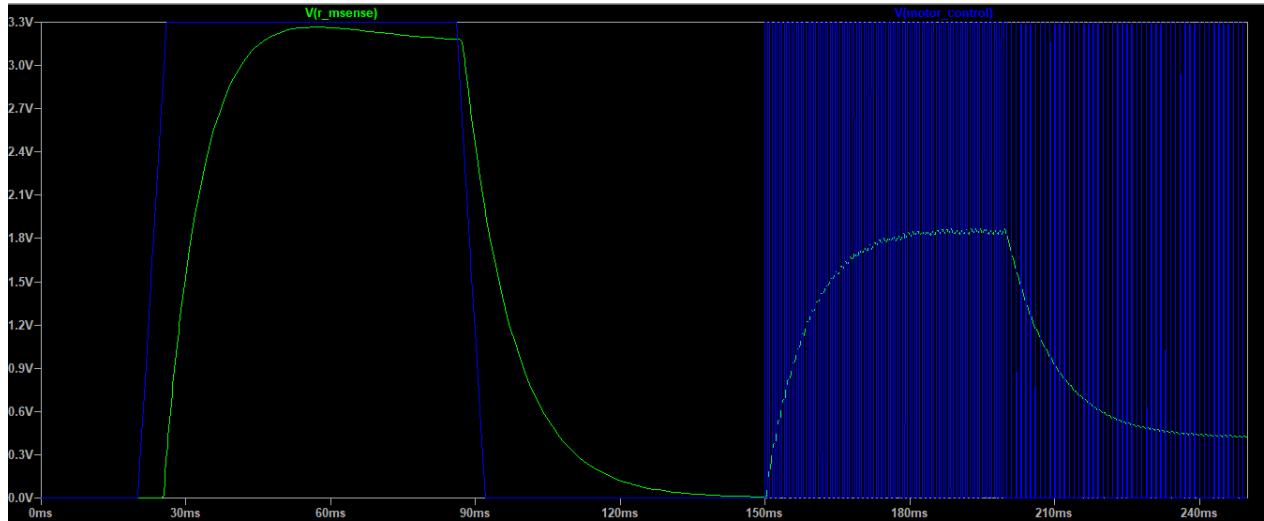


Figure 3.11: Simulated results

3.6.2. Measured results

The circuit was implemented and the measurements can be seen in 3.4

Speed	Output measured
fast	3.32
slow	1.59
No movement	0.50

Table 3.4: Output values of the analogue circuit

3.7. Battery protection

3.7.1. simulated results

3.7.2. Measured results

Table 3.5: Measured results for under voltage protection

Battery	Load	Switch
6.0 V	6.0V	on
5.96 V	0V	off
6.2 V	0V	off
6.21V	6.22V	on

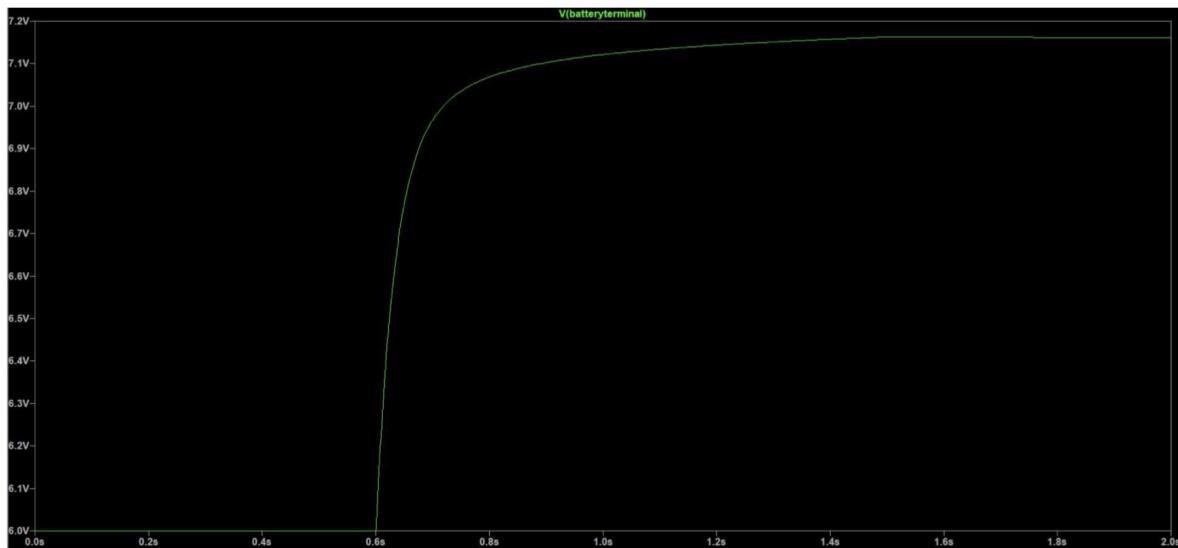


Figure 3.12: Simulated results

3.8. Lead-acid battery results

3.8.1. Simulated results

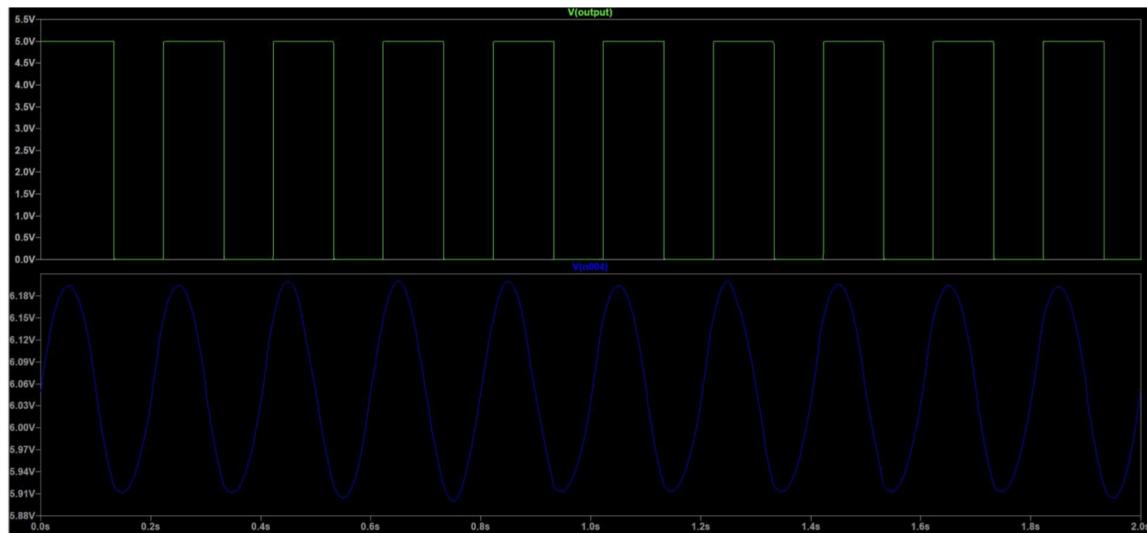


Figure 3.13: Simulated results

3.8.2. Measured results charger

The charger what setup and the output was measured by a multimeter to obtain the following values in table 3.6

Resistance	Output measured
1K Ω	7.28V
50 Ω	6.56V

Table 3.6: Output values

3.9. Bluetooth Serial Interface

Bluetooth was used by implementing the Bluetooth serial port the following results were obtained.

Left wheel instruction :15 Left wheel current (mA): 165 Left sensor range (m): 1.01 Right wheel instruction: 0 Right wheel current(mA):23 Right sensor range (m):0.44 Battery voltage (V): 7.2	Left wheel instruction :0 Left wheel current (mA): 12 Left sensor range (m): 0.43 Right wheel instruction: 15 Right wheel current(mA):165 Right sensor range (m):1.01 Battery voltage (V): 7.2	Left wheel instruction :11 Left wheel current (mA): 3 Left sensor range (m): 0.39 Right wheel instruction: 11 Right wheel current(mA):10 Right sensor range (m):0.43 Battery voltage (V): 7.2
(a) Right turn	(b) Left turn	(c) Object in front of both sensors

Left wheel instruction :15 Left wheel current (mA): 170 Left sensor range (m): 1 Right wheel instruction: 15 Right wheel current(mA):168 Right sensor range (m):1 Battery voltage (V): 7.2	(d) No object in front of the sensor
--	--------------------------------------


Figure 3.14: The outputs read from Termite

3.10. GUI Results


In the main menu that can be seen in Fig.3.15b the Comms that the user wants to use can be chosen. All the options can also be seen in the given window. In the Telemetry Window in Fig 3.15c all the needed information can be seen. In the Remote control window all the buttons can be seen that the user can use to control the car. The control window can be seen in the below fig 3.15a.



[] (a) Remote Control Window

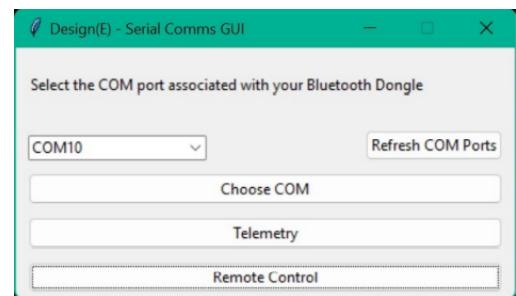

(b) SerialComms or the main menu

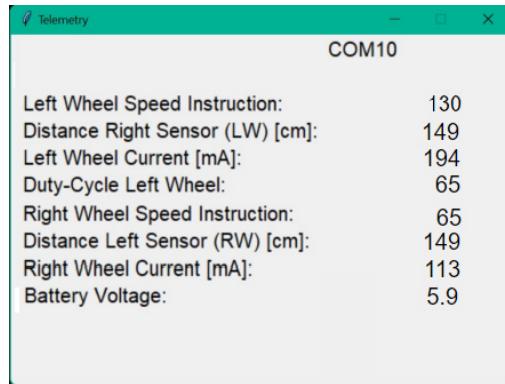

(c) Telemetry Window

Figure 3.15: The outputs produced by the implemented GUI

Chapter 4

Physical implementation

Figure 4.1: Picture of circuit and Student card

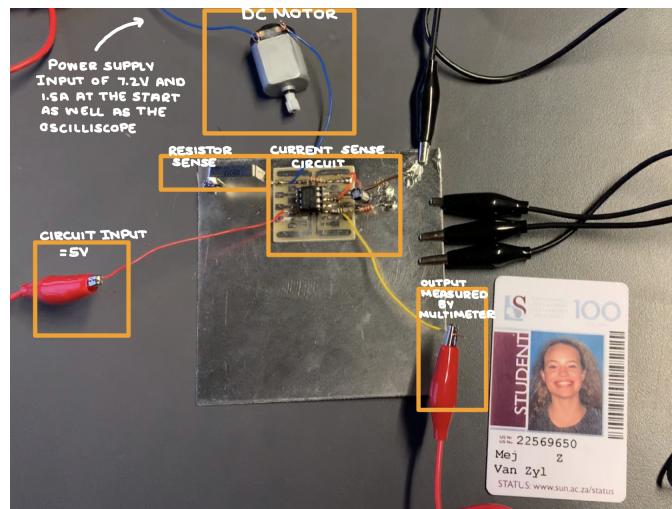


Figure 4.2: Picture of circuit and set-up in the labs

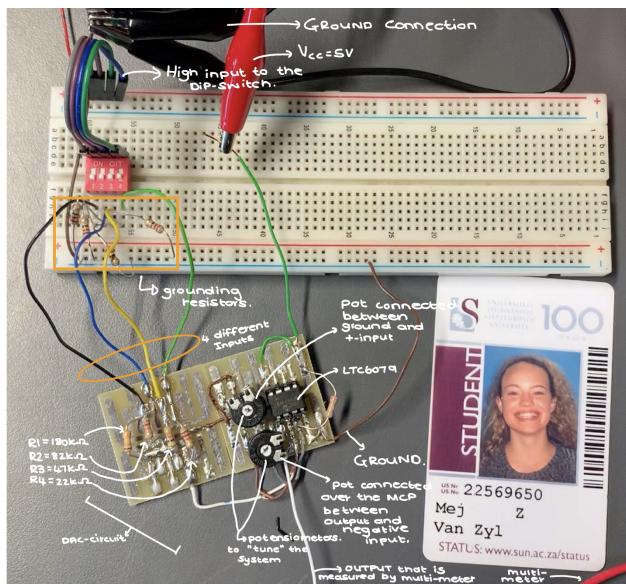


Figure 4.3: Student card and DAC Circuit

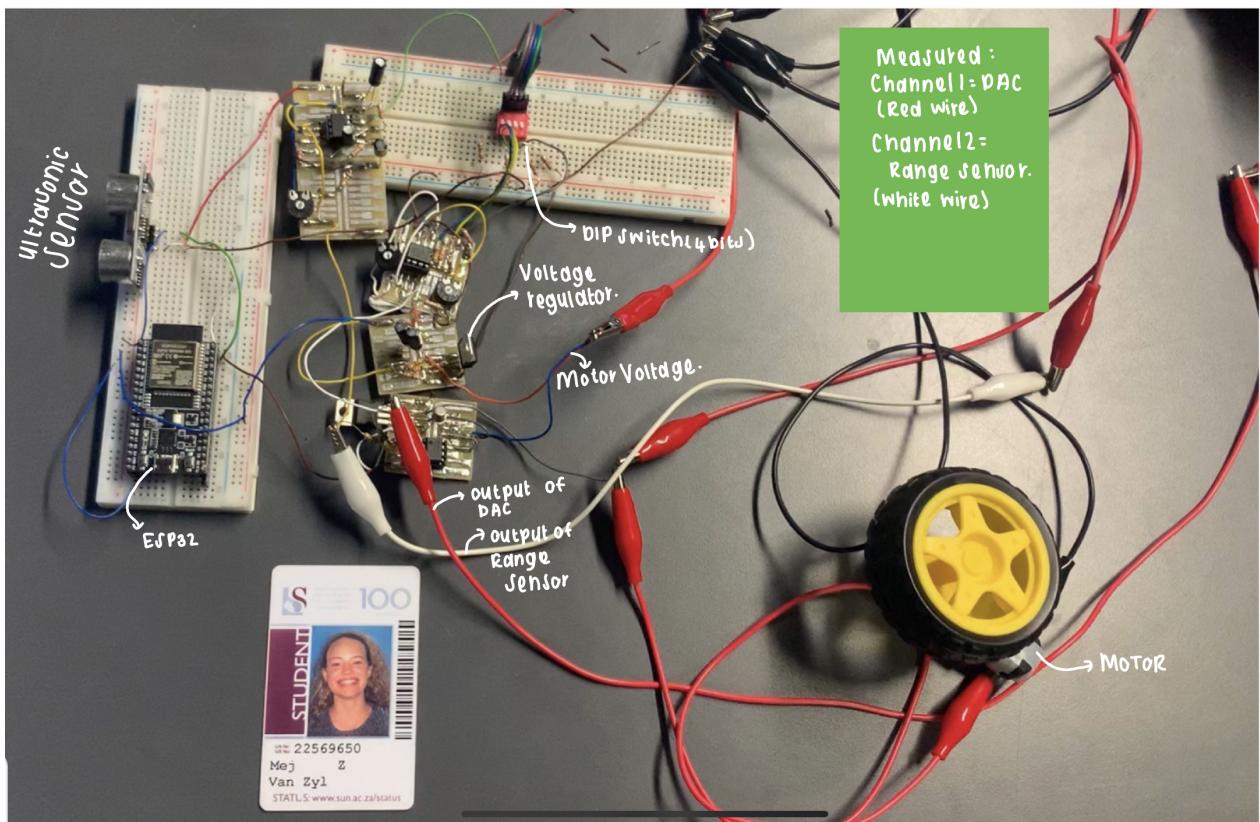


Figure 4.4: A4 circuit

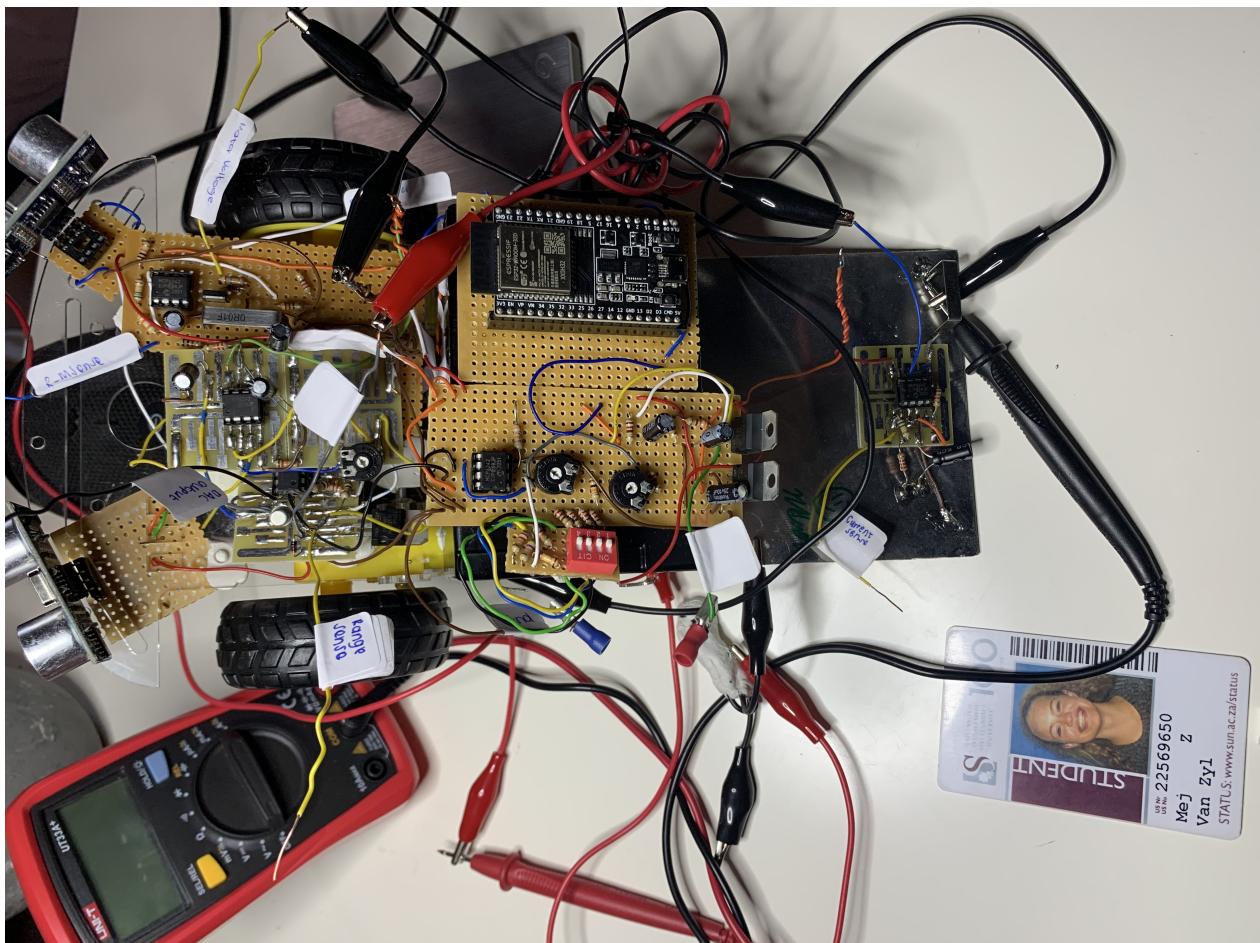


Figure 4.5: A5 circuit

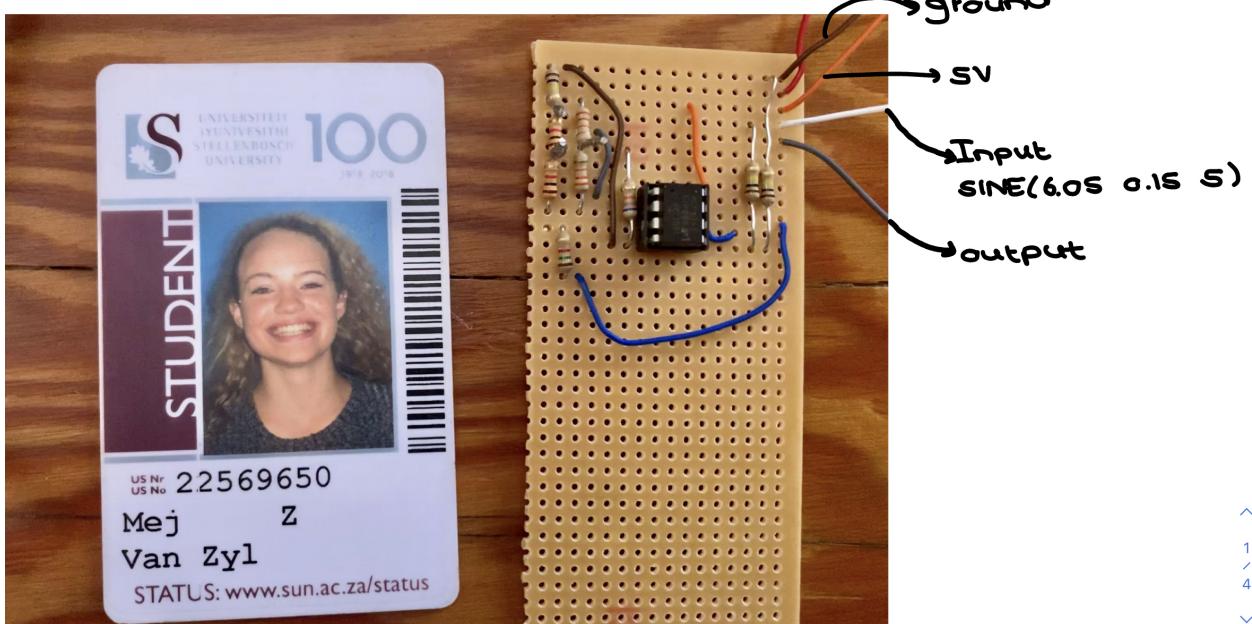


Figure 4.6: Under Voltage circuit

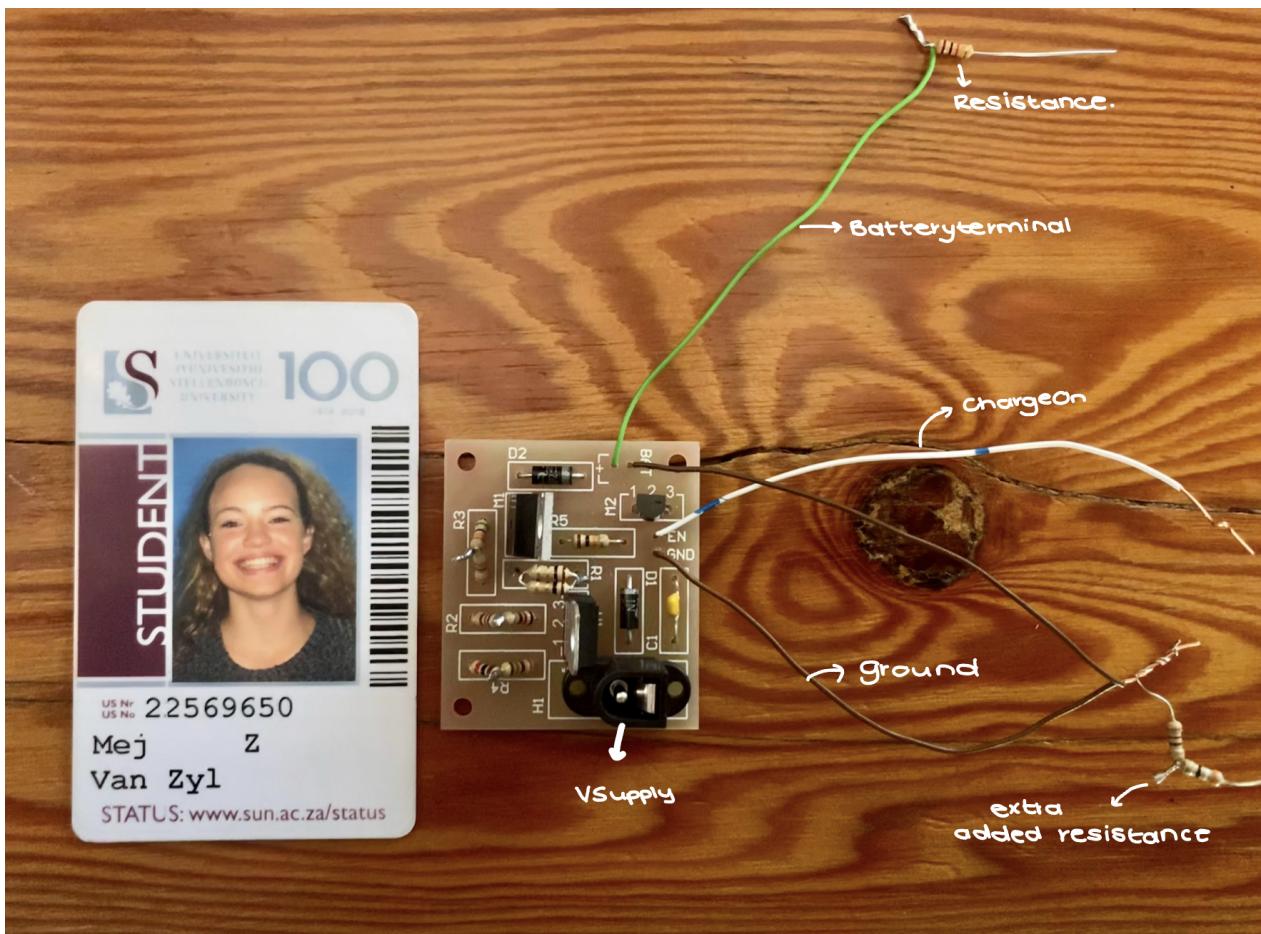


Figure 4.7: Battery charger circuit

Bibliography

- [1] BBC, “How to make opamps amp op,” 2018. [Online]. Available: www.electronics-tutorials.ws
- [2] Microchip Technology Inc., “Microchip mcp6241/1r/1u/2/4,” 2008. [Online]. Available: <https://ww1.microchip.com/downloads/aemDocuments/documents/OTH/ProductDocuments/DataSheets/21882d.pdf>

Appendix A

Social contract



UNIVERSITEIT•STELLENBOSCH•UNIVERSITY
jou kennisvenoot • your knowledge partner

E-design 344 Social Contract

2021

The purpose of this document is to establish commitment between the student and the organisers of E344. Beyond the commitment made here, it is not binding.

In the months preceding the term, the lecturer (Thinus Booyens) and the Teaching Assistant (Kurt Coetzer) spent countless hours to prepare for E344 to ensure that you get your money's worth and that you are enabled to learn from the module and demonstrate and be assessed on your skills. We commit to prepare the assignments, to set the tests and assessments fairly, to be reasonably available, and to provide feedback and support as best and fast we can. We will work hard to give you the best opportunity to learn from and pass analogue electronic design E344.

I, have registered for E344 of my own volition with the intention to learn of and be assessed on the principals of analogue electronic design. Despite the potential publication online of supplementary videos on specific topics, I acknowledge that I am expected to attend the scheduled lectures to make the most of these appointments and learning opportunities. Moreover, I realise I am expected to spend the additional requisite number of hours on E344 as specified in the yearbook.

I acknowledge that E344 is an important part of my journey to becoming a professional engineer, and that my conduct should be reflective thereof. This includes doing and submitting my own work, working hard, starting on time, and assimilating as much information as possible. It also includes showing respect towards the University's equipment, staff, and their time.

Prof. MJ Booyens

Student number: 22569650

Signature: A handwritten signature of Prof. MJ Booyens.

Digitally signed by MJ
BOOYSEN
Date: 2021-07-29
16:46:05 +0200

Signature: A handwritten signature of Kurt Coetzer.

Date: 29 July 2021

Date: 22/07/2022

Appendix B

GitHub Activity Heatmap

